

ECE/CS 250: Computer Architecture

Combinational Logic: Boolean Algebra, Logic Gates


Copyright Daniel Sorin
Duke University

Slides are derived from work by
Drew Hilton (Duke), Alvy Lebeck (Duke), Amir
Roth (Penn)

Reading

- **Appendix B (parts 1,2,3,5,6,7,8,9,10)**
- **This material is covered in MUCH greater depth in ECE/CS 350 – please take ECE/CS 350 if you want to learn enough digital design to build your own processor**

What We've Done, Where We're Going

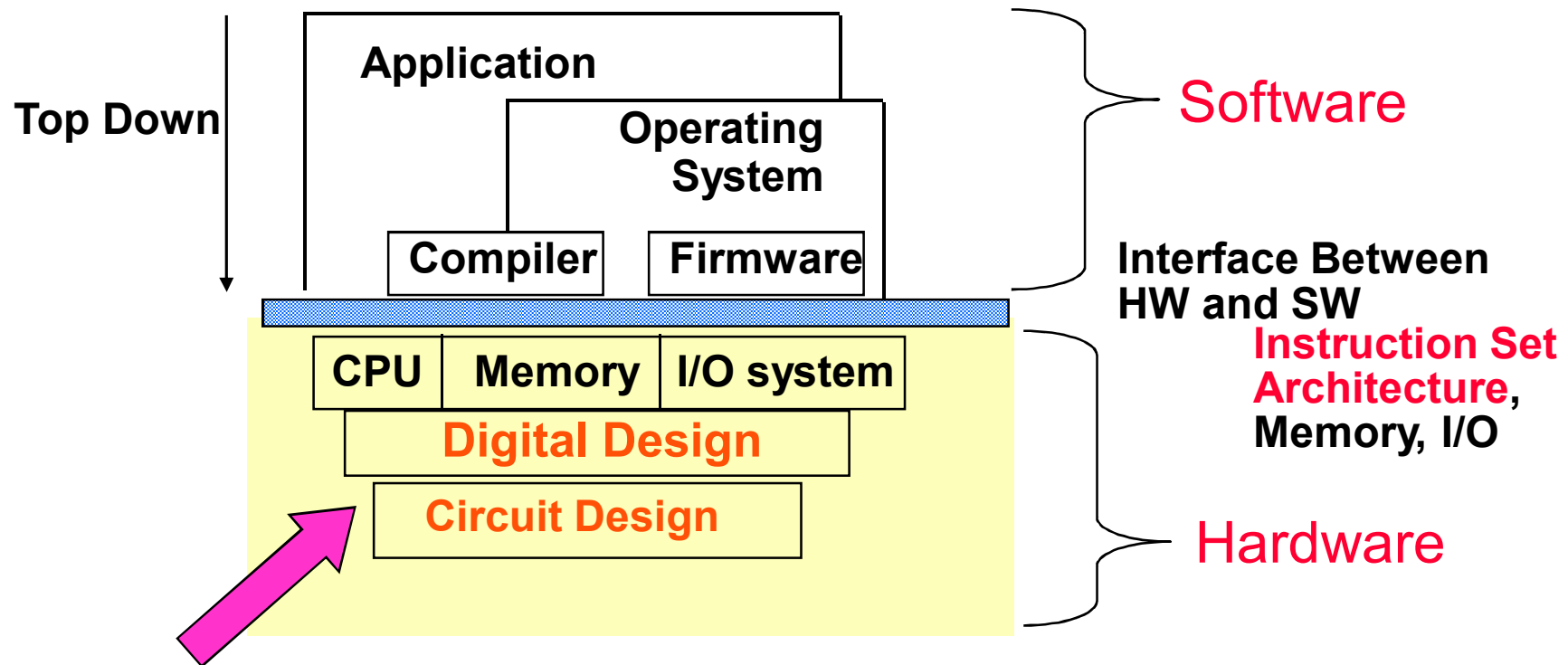

(Almost) Bottom UP to CPU

Computer = Machine That Manipulates Bits

- **Everything is in binary (bunches of 0s and 1s)**
 - Instructions, numbers, memory locations, etc.
- **Computer is a machine that operates on bits**
 - Executing instructions → operating on bits
- **Computers physically made of transistors**
 - Electrically controlled switches
- **We can use transistors to build logic**
 - E.g., if this bit is a 0 and that bit is a 1, then set some other bit to be a 1
 - E.g., if the first 5 bits of the instruction are 10010 then set this other bit to 1 (to tell the adder to subtract instead of add)

How Many Transistors Are We Talking About?

Pentium III

- Processor Core 9.5 Million Transistors
- **Total: 28 Million Transistors**

Pentium 4

- **Total: 42 Million Transistors**

Core2 Duo (two processor cores)

- **Total: 290 Million Transistors**

Core2 Duo Extreme (4 processor cores, 8MB cache)

- **Total: 590 Million Transistors**

Core i7 with 6-cores

- **Total: 2.27 Billion Transistors**

How do they design such a thing? Carefully!

Abstraction!

- Use of **abstraction** (key to design of any large system)
 - Put a few (2-8) transistors into **logic gate** (OR, AND, XOR, ...)
 - Combine gates into logical functions (add, select,....)
 - Combine adders, shifters, etc., together into modules
 - Units with well-defined interfaces for large tasks: e.g., decode
 - Combine a dozen of those into a core...
 - Stick 4 cores on a chip...

You are here:

- Use of **abstraction** (key to design of any large system)
 - Put a few (2-8) transistors into a **logic gate**
 - **Combine gates into logical functions (add, select,...)**
 - Combine adders, muxes, etc together into modules
 - Units with well-defined interfaces for large tasks: e.g., decode
 - Combine a dozen of those into a core...
 - Stick 4 cores on a chip...

Boolean Algebra

- **First step to logic: Boolean Algebra**
 - Manipulation of True / False (1/0)
 - After all: everything is just 1s and 0s
- **Given inputs (variables): A, B, X, P, Q...**
 - Compute outputs using logical operators, such as:
- **NOT:** $\neg A$ ($= \sim A = \bar{A}$)
- **AND:** $A \& B$ ($= A \cdot B = A * B = AB = A \wedge B$) = `A&&B` in C/C++
- **OR:** $A \mid B$ ($= A + B = A \vee B$) = `A || B` in C/C++
- **XOR:** $A \wedge B$ ($= A \oplus B$)
- NAND, NOR, XNOR, Etc.

Truth Tables

- Can represent as **Truth Table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

Truth Tables

- Can represent as **truth table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND (a , b)
0	0	0
0	1	0
1	0	0
1	1	1

Truth Tables

- Can represent as **truth table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND (a , b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR (a , b)
0	0	0
0	1	1
1	0	1
1	1	1

Truth Tables

- Can represent as **truth table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND (a , b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR (a , b)
0	0	0
0	1	1
1	0	1
1	1	1

a	b	XOR (a , b)
0	0	0
0	1	1
1	0	1
1	1	0

a	b	NAND (a , b)
0	0	1
0	1	1
1	0	1
1	1	0

a	b	NOR (a , b)
0	0	1
0	1	0
1	0	0
1	1	0

Any Inputs, Any Outputs

- Can have any # of inputs, any # of outputs
- Can have arbitrary functions:

a	b	c	f_1	f_2
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	1	1

Let's Write a Truth Table for a Function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT
Column Per Input
Column Per Output

A	B	C	Output

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

A	B	C	Output
0	0	0	

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

A	B	C	Output
0	0	0	
0	0	1	

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

A	B	C	Output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

Compute Output

$(0 \& 0) \mid !0 = 0 \mid 1 = 1$

A	B	C	Output
0	0	0	1
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

Compute Output

$$(0 \& 0) \mid !1 = 0 \mid 0 = 0$$

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

Compute Output

$(0 \& 1) \mid !0 = 0 \mid 1 = 1$

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Let's write a Truth Table for a function...

- **Example:**
 $(A \& B) \mid !C$

Start with Empty TT

Column Per Input

Column Per Output

Fill in Inputs

Counting in Binary

Compute Output

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

You try one...

- **Try one yourself (take 2 minutes):**
 $(\neg A \mid B) \ \& \ \neg C$

Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm..

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm ...

Could write down every “true” case

Then OR together:

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$

$(\neg A \ \& \ \neg B \ \& \ C) \mid$

$(\neg A \ \& \ B \ \& \ \neg C) \mid$

$(A \ \& \ B \ \& \ \neg C) \mid$

$(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm..

Could write down every “true” case

Then OR together:

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$

$(\neg A \ \& \ \neg B \ \& \ C) \mid$

$(\neg A \ \& \ B \ \& \ \neg C) \mid$

$(A \ \& \ B \ \& \ \neg C) \mid$

$(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm..

Could write down every “true” case

Then OR together:

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$

$(\neg A \ \& \ \neg B \ \& \ C) \mid$

$(\neg A \ \& \ B \ \& \ \neg C) \mid$

$(A \ \& \ B \ \& \ \neg C) \mid$

$(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach is called “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$
 $(A \ \& \ B \ \& \ \neg C) \mid$
 $(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach: “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

(!A & !B & !C) |

(!A & !B & C) |

(!A & B & !C) |

(A & B & !C) |

(A & B & C)

Could just be (A & B) here ?

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach: “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

(!A & !B & !C) |

(!A & !B & C) |

(!A & B & !C) |

(A&B)

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach: “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

(!A & !B & !C) |

(!A & !B & C) |

(!A & B & !C) |

(A&B)

Could just be (!A & !B) here

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach: “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

$(\neg A \ \& \ \neg B) \mid$
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$
 $(A \ \& \ B)$

Looks nicer...

Can we do better?

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach: “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

$(\neg A \ \& \ \neg B) \mid$
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$
 $(A \ \& \ B)$

This has a lot in common:
 $\neg A \ \& \ (\text{something})$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Suppose I turn it around...

- This approach: “sum of products”
 - Works every time
 - Result is right...
 - But really ugly

$(\neg A \ \& \ \neg (B \ \& \ C)) \mid$
 $(A \ \& \ B)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Just did some of these by intuition.. but

- Somewhat intuitive approach to simplifying
- This is **math**, so there are formal rules
 - Just like “regular” algebra

Boolean Function Simplification

- Boolean expressions can be simplified by using the following rules (bitwise logical):

- $A \ \& \ A = A$

- $A \ \& \ 0 = 0$

- $A \ \& \ 1 = A$

- $A \ \& \ !A = 0$

- $A \ | \ A = A$

- $A \ | \ 0 = A$

- $A \ | \ 1 = 1$

- $A \ | \ !A = 1$

- $!!A = A$

- $\&$ and $|$ are both commutative and associative

- $\&$ and $|$ can be distributed: $A \ \& \ (B \ | \ C) = (A \ \& \ B) \ | \ (A \ \& \ C)$

- $\&$ and $|$ can be subsumed: $A \ | \ (A \ \& \ B) = A$

DeMorgan's Laws

- **Two (less obvious) Laws of Boolean Algebra:**
 - Let's push negations inside, flipping & and |

$$\mathbf{!(A \ \& \ B) \ = \ (!A) \ | \ (!B)}$$

$$\mathbf{!(A \ | \ B) \ = \ (!A) \ \& \ (!B)}$$

- You should try this at home – build truth tables for both the left and right sides and see that they're the same

Using DeMorgan on Early Example

$$\begin{aligned} & (!A \ \& \ ! (B \ \& \ C)) \ | \\ & (A \ \& \ B) \\ \\ = \\ & (!A \ \& \ (!B \ | \ !C)) \ | \\ & (A \ \& \ B) \end{aligned}$$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$

Simplification Example:

$\neg (\neg A \mid \neg (A \& (B \mid C)))$

DeMorgan's

$\neg \neg A \& \neg \neg (A \& (B \mid C))$

Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$

DeMorgan's

$\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$

Double Negation Elimination

$A \ \& \ (A \ \& \ (B \mid C))$

Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$

DeMorgan's

$\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$

Double Negation Elimination

$A \ \& \ (A \ \& \ (B \mid C))$

Associativity of &

$(A \ \& \ A) \ \& \ (B \mid C)$

Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$

DeMorgan's

$\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$

Double Negation Elimination

$A \ \& \ (A \ \& \ (B \mid C))$

Associativity of &

$(A \ \& \ A) \ \& \ (B \mid C)$

$A \ \& \ A = A$

$A \ \& \ (B \mid C)$

You try this:

Come up with a formula for this Truth Table

Simplify as much as possible

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Something That Trips Up Students

!A&!B is not the same as !(AB)

Students tend to notice this when it's written this way but NOT when it's written with lines above the terms:

$$\overline{A} \cdot \overline{B} \neq \overline{AB}$$

“Not A and Not B” is not the same as “Not AB”

The former is true if (A,B) = (0,0).

The latter is true if (A,B) = (0,0) or (0,1) or (1,0).








Applying the Theory

- **Lots of good theory**
- **Can reason about complex Boolean expressions**
- **But why is this useful? (fun party trick)**

Boolean Gates


- **Gates** are electronic devices that implement simple Boolean functions (building blocks of hardware)

Examples

       


Guide to Remembering your Gates

 - This one looks like it just points its input where to go
 - It just produces its input as its output
 - Called a buffer




Guide to Remembering your Gates

 
- This one looks like it just points its input where to go
 - It just produces its input as its output
 - Called a buffer




- A circle always means negate (invert)

 

Brief Interlude: Building An Inverter

 


This is not on the test.

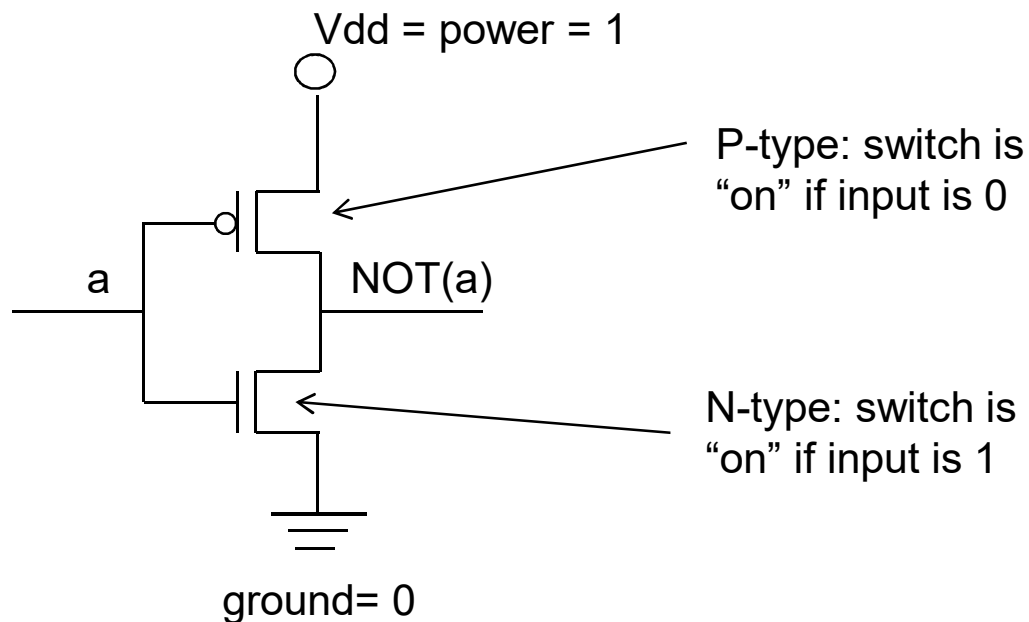


Guide to Remembering Your Gates

 - **AND Gates have a straight edge, like an A (in AND)**





 OR Gates have a curved edge, like an O (in OR)





Guide to Remembering Your Gates

- If we stick a circle on them...

  


Circle = NOT

  


- We get NAND (NOT-AND) and NOR (NOT-OR)
 - $\text{NAND}(a, b) = \text{NOT}(\text{AND}(a, b))$

Guide to Remembering Your Gates

 - **XOR looks like OR (curved line)**
 - But has two lines (like an X does)



 
- **Can put a dot for XNOR**
 - XNOR is 1-bit “equals” by the way



Boolean Functions, Gates and Circuits


- **Circuits** are made from a network of gates.

$$(!A \ \& \ !C) \mid (A \ \& \ C)$$

 

A few more words about gates

 - **Gates have inputs and outputs**
 - If you try to hook up two outputs, bad things happen (your processor catches fire)



- If you don't hook up an input, it behaves kind of randomly (also not good, but not set-your-chip-on-fire bad)

Let's Make a Useful Circuit

- **Pick between 2 inputs (called 2-to-1 MUX)**
 - Short for multiplexor
- **What might we do first?**

Let's Make a Useful Circuit

- **Pick between 2 inputs (called 2-to-1 MUX)**
 - Short for multiplexor
- **What might we do first?**
 - Make a truth table?
 - S is selector:
 - S=0, pick A
 - S=1, pick B

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Let's Make a Useful Circuit

- **Pick between 2 inputs (called 2-to-1 MUX)**
 - Short for multiplexor

- **What might we do first?**

- Make a truth table?

- S is selector:

- S=0, pick A

- S=1, pick B

- **Next: sum-of-products**

$(\neg A \ \& \ B \ \& \ S) \mid$

$(A \ \& \ \neg B \ \& \ \neg S) \mid$

$(A \ \& \ B \ \& \ \neg S) \mid$

$(A \ \& \ B \ \& \ S)$

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


Let's Make a Useful Circuit

- **Pick between 2 inputs (called 2-to-1 MUX)**
 - Short for multiplexor
- **What might we do first?**
 - Make a truth table?
 - S is selector:
 - S=0, pick A
 - S=1, pick B
- **Next: sum-of-products**
- **Simplify**
 $(A \ \& \ !S) \mid$
 $(B \ \& \ S)$


A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Circuit Example: 2x1 MUX


Draw it in gates:

 

So common, we give it
its own symbol:

 

Example 4x1 MUX

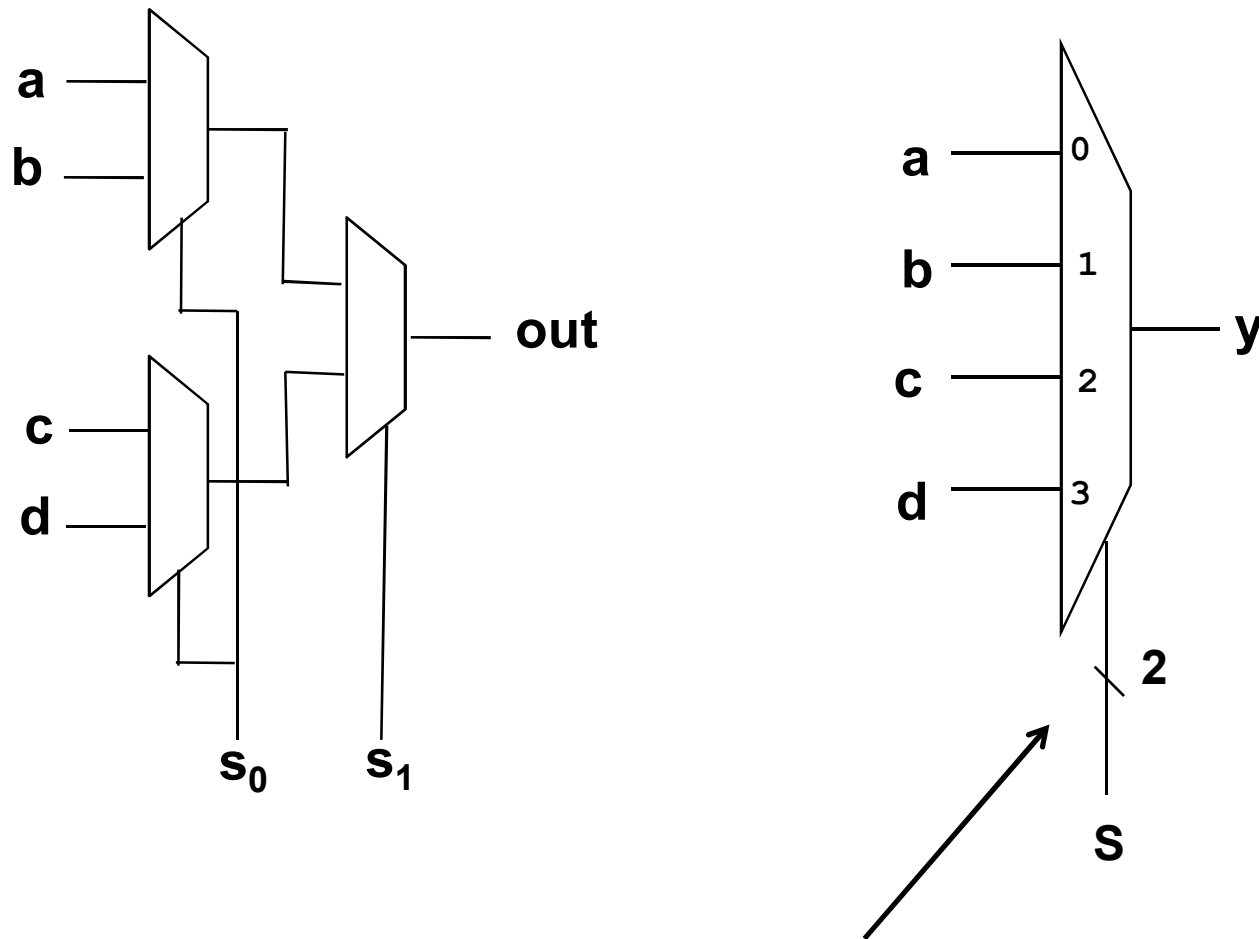


The / 2 on the wire means "2 bits"

Arithmetic and Logical Operations in ISA

- What operations are there?
- How do we implement them?
 - Consider a 1-bit Adder


A 1-bit Full Adder

 

$$\begin{array}{r}
 01101100 \\
 01101101 \\
 +00101100 \\
 \hline
 10011001
 \end{array}$$

a	b	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Example: 4-bit adder

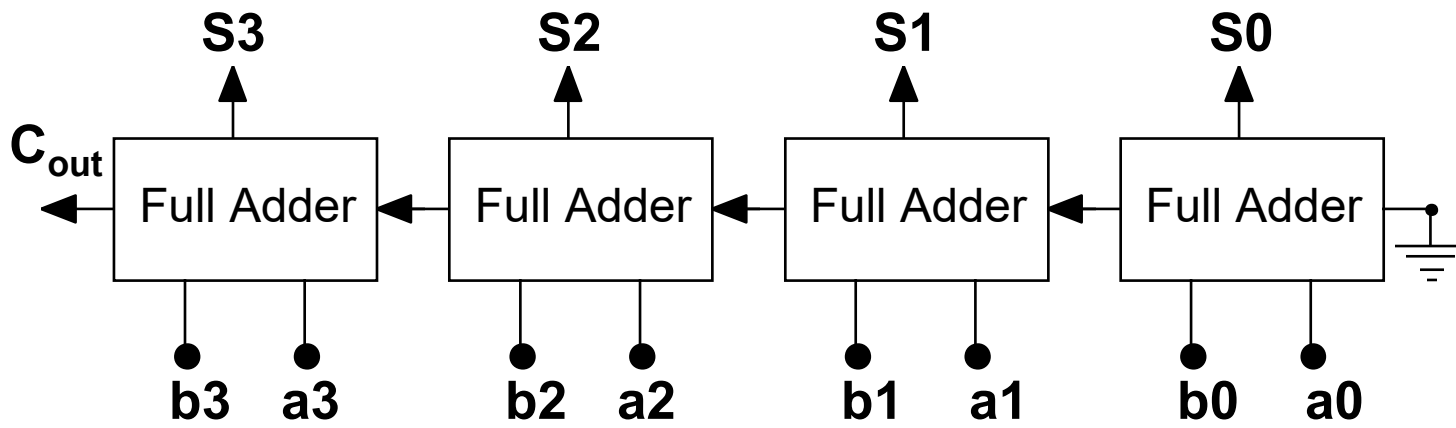

Subtraction

- How do we perform integer subtraction?
- What is the hardware?
 - Recall: hardware was why 2's complement was good idea


- Remember: Subtraction is just addition

$$X - Y =$$

$$X + (-Y) =$$

$$X + (\sim Y + 1)$$


Example: Adder/Subtractor

 


Overflow

- **We can detect unsigned overflow by looking at CO**
- **How would we detect signed overflow?**
 - If adding positive numbers and result “is” negative
 - If adding negative numbers and result “is” positive
 - At most significant bit of adder, check if $CI \neq CO$
 - Can check with XOR gate


Add/Subtract With Overflow Detection

 

ALU Slice

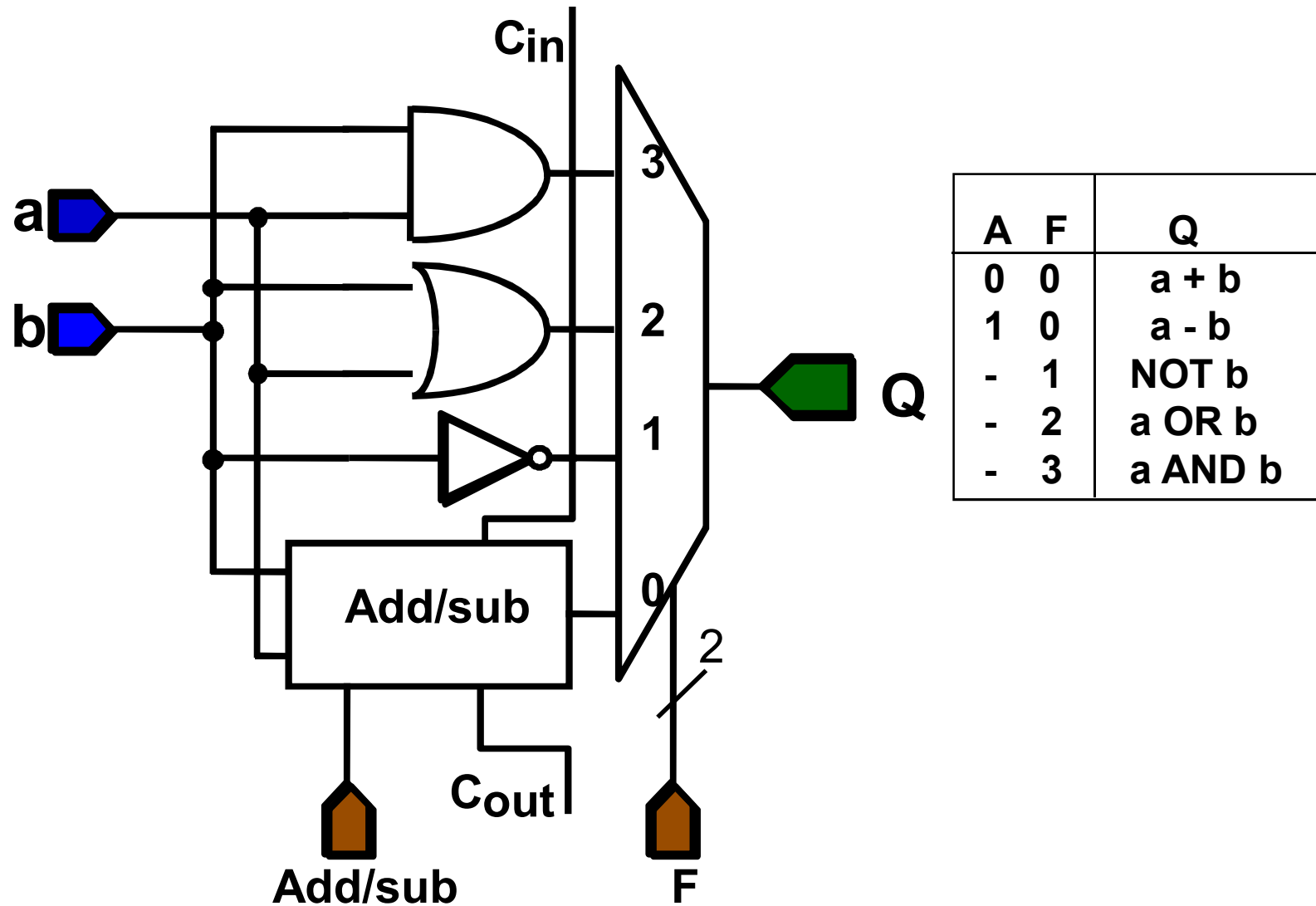


The ALU

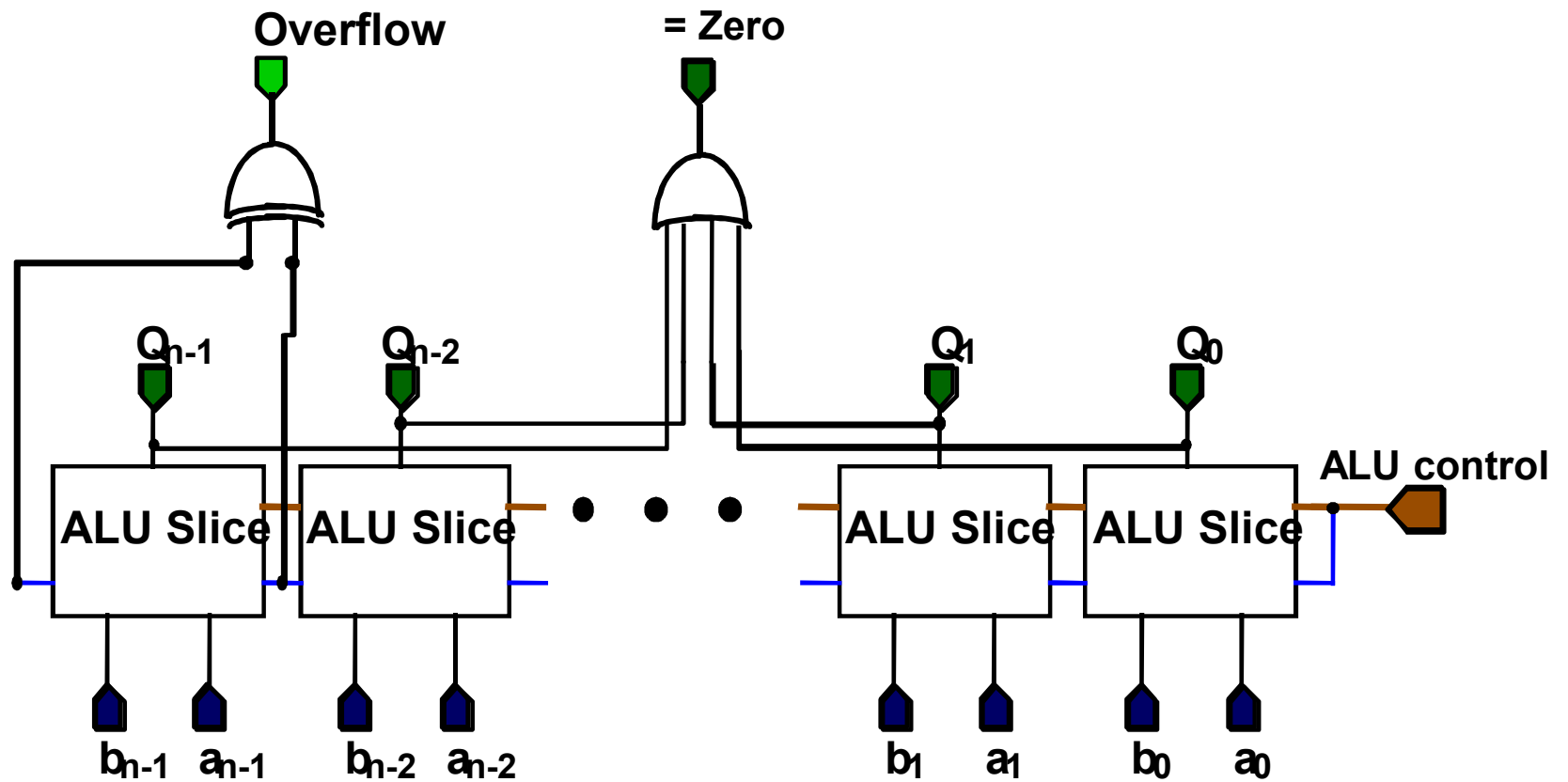

Abstraction: The ALU

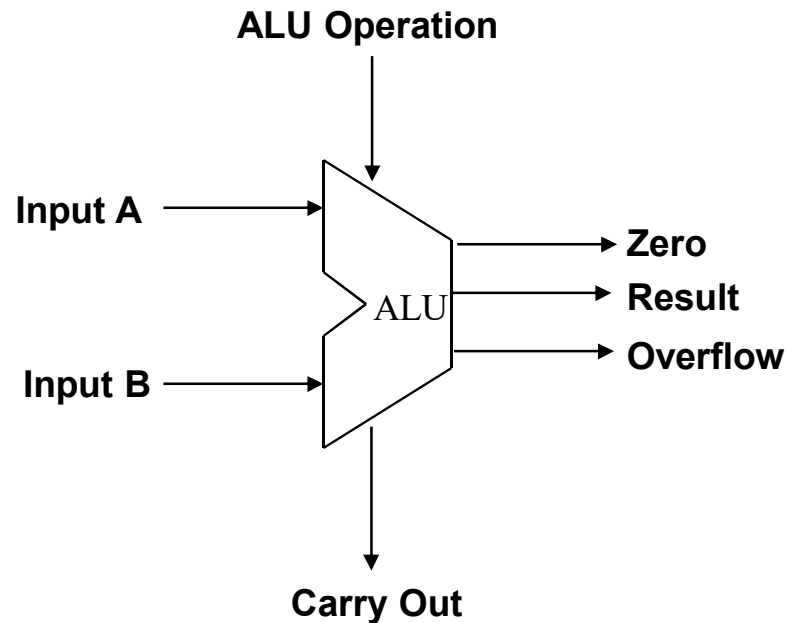- **General structure**
- **Two operand inputs**
- **Control inputs**
- **We can build circuits for**
 - **Multiplication**
 - **Division**
 - **They are more complex (ECE/CS 350)**




Another Operation We Might Want: Shift

- Remember the << and >> operations?
 - Shift left/shift right?
 - How would we implement these?
- Suppose you have an 8-bit number
 $b_7b_6b_5b_4b_3b_2b_1b_0$
- And you can shift it left by a 3-bit number
 $s_2s_1s_0$
- Option 1: Truth Table?
 - $2^{11} = 2048$ rows? Yuck.


Let's simplify to 1-bit left-shift

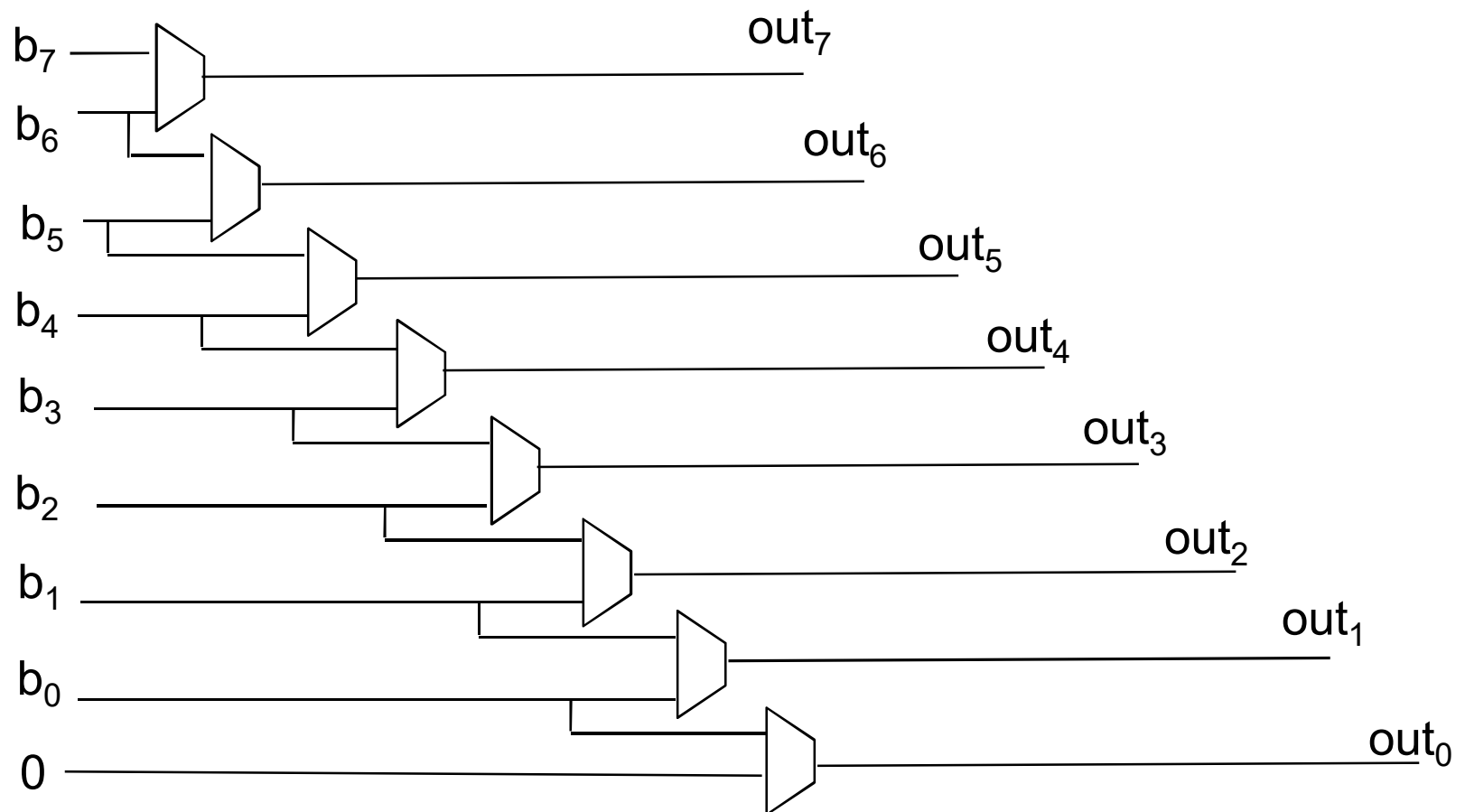- **Simpler problem: 8-bit number left-shifted by 1 bit number (shift amount selects each mux)**




Let's simplify to 2-bit left shift

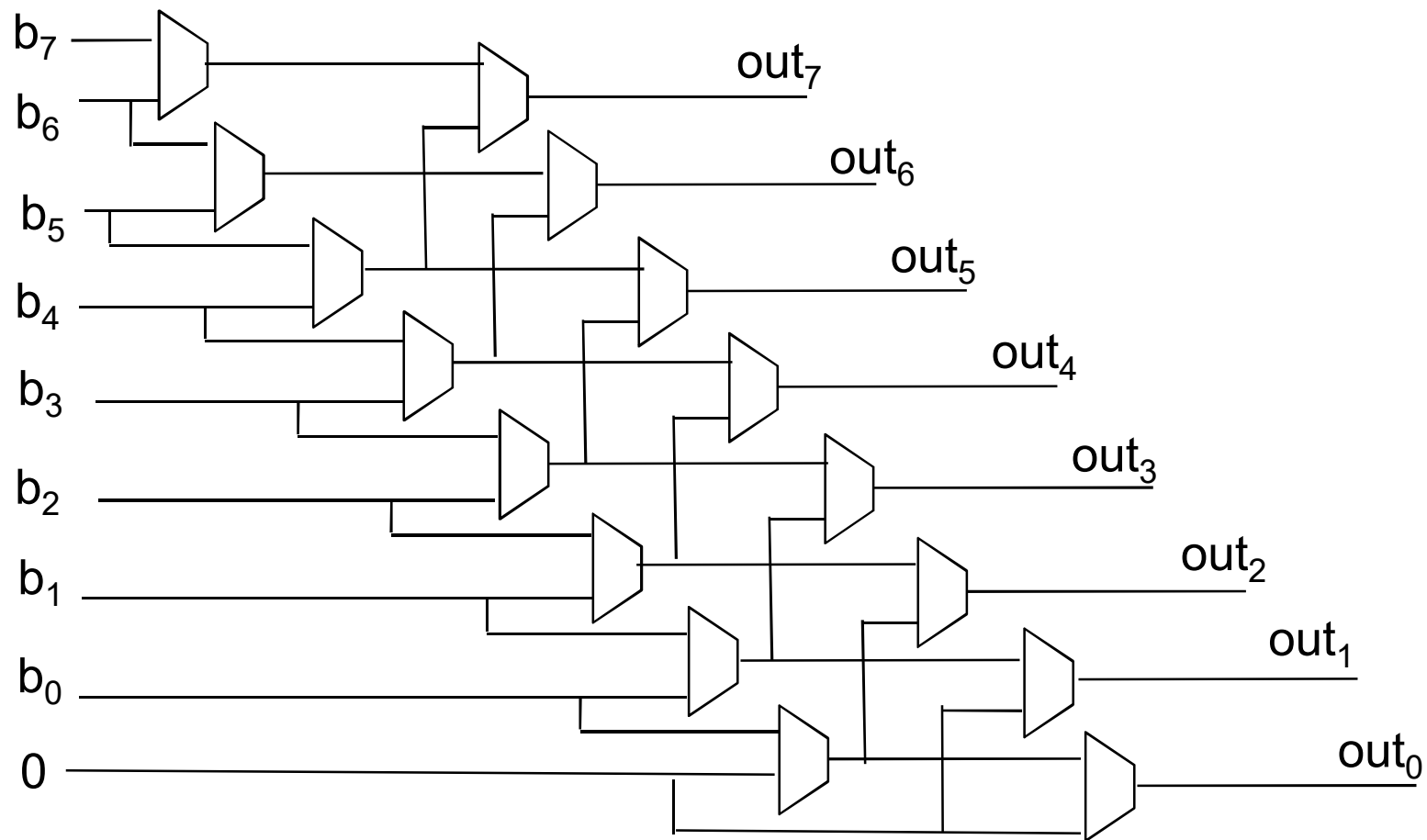- **Simpler problem: 8-bit number left-shifted by 2 bit number (i.e., can left-shift by 0, 1, 2, or 3)**




Now left-shifted by 3-bit number

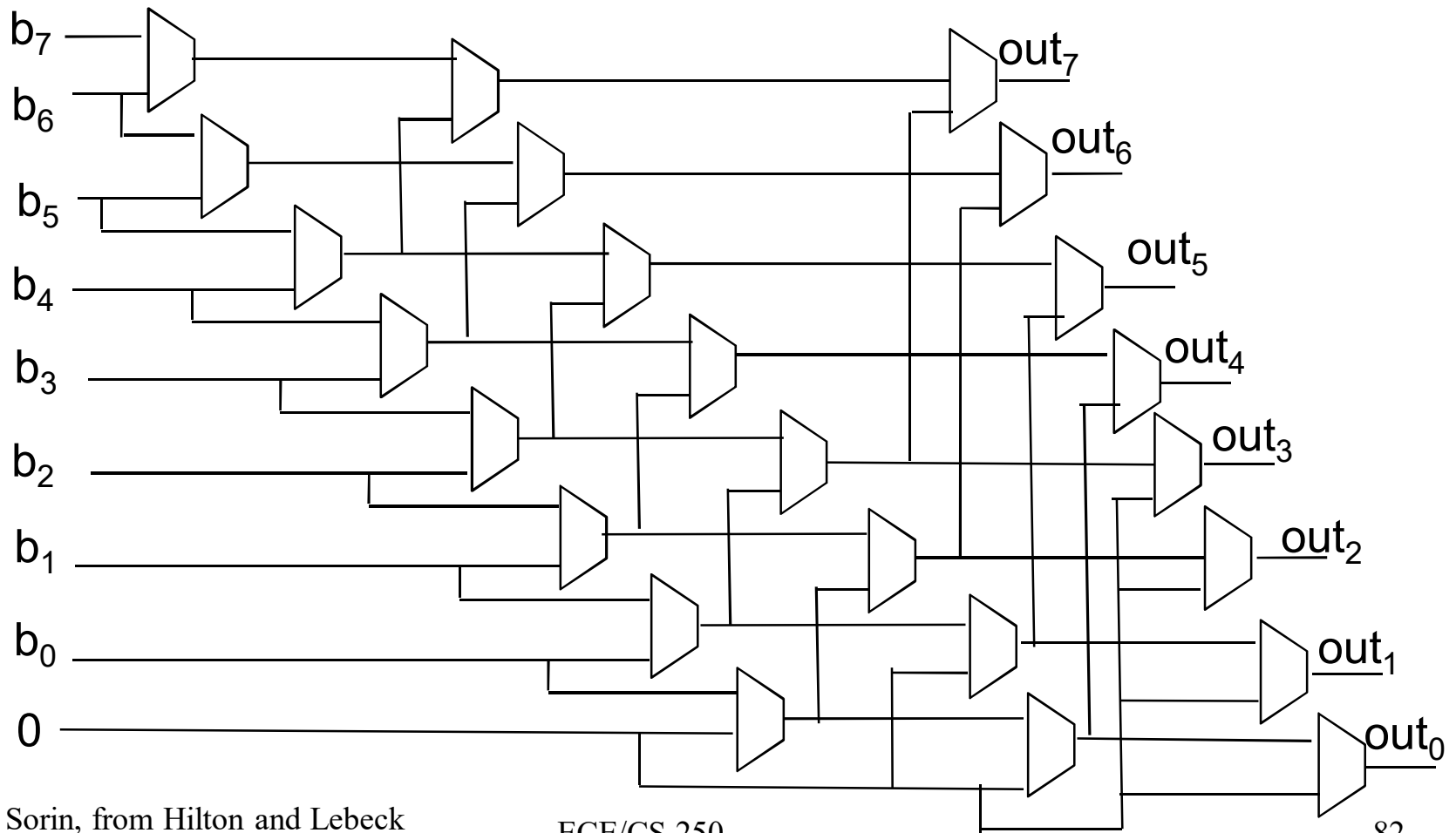- Full problem: 8-bit number left-shifted by 3 bit number (can shift by 0-7 bits)




Now shifted by 3-bit number

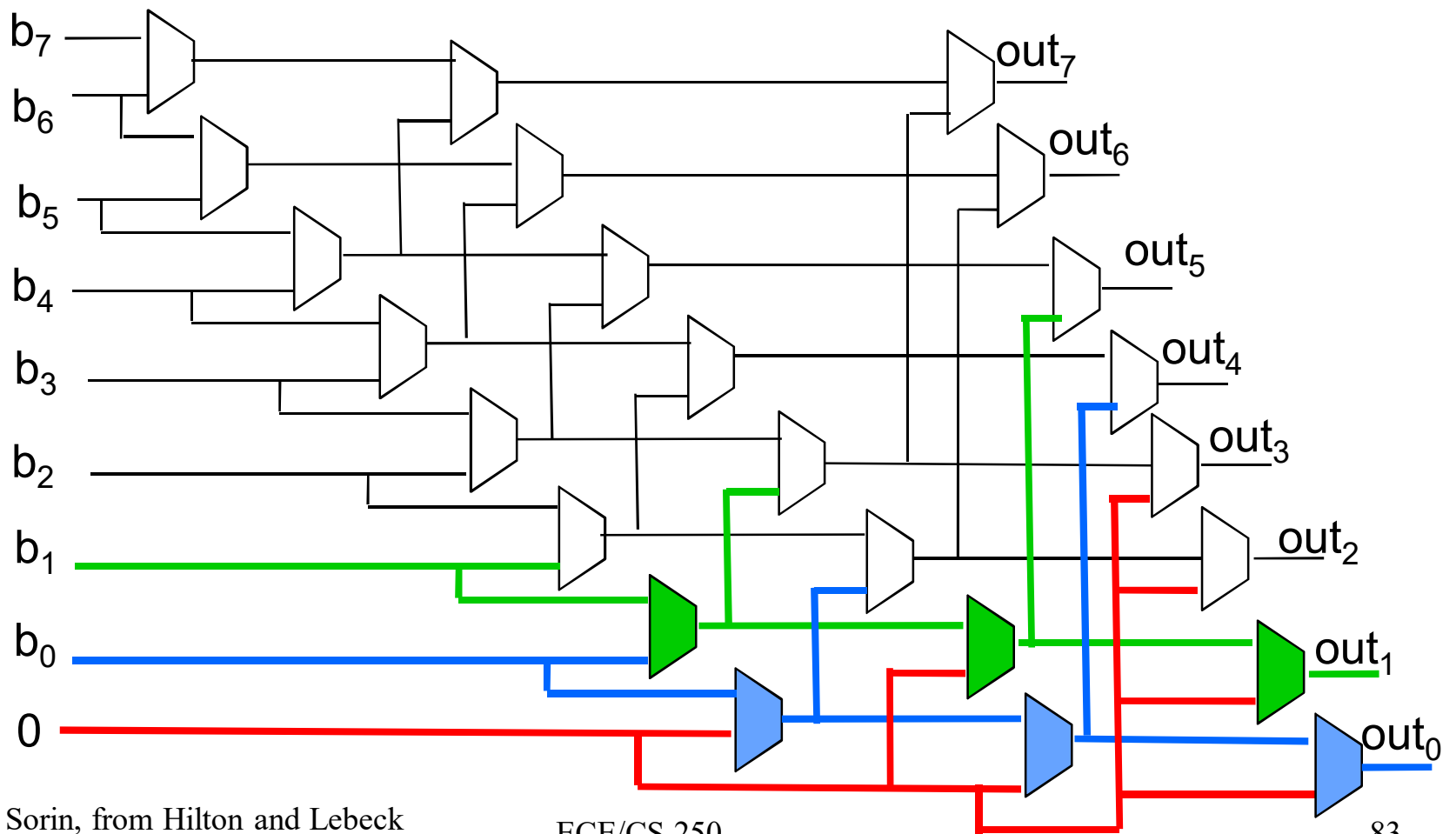- **Shifter in action: shift by 000 (all muxes have S=0)**




Now shifted by 3-bit number

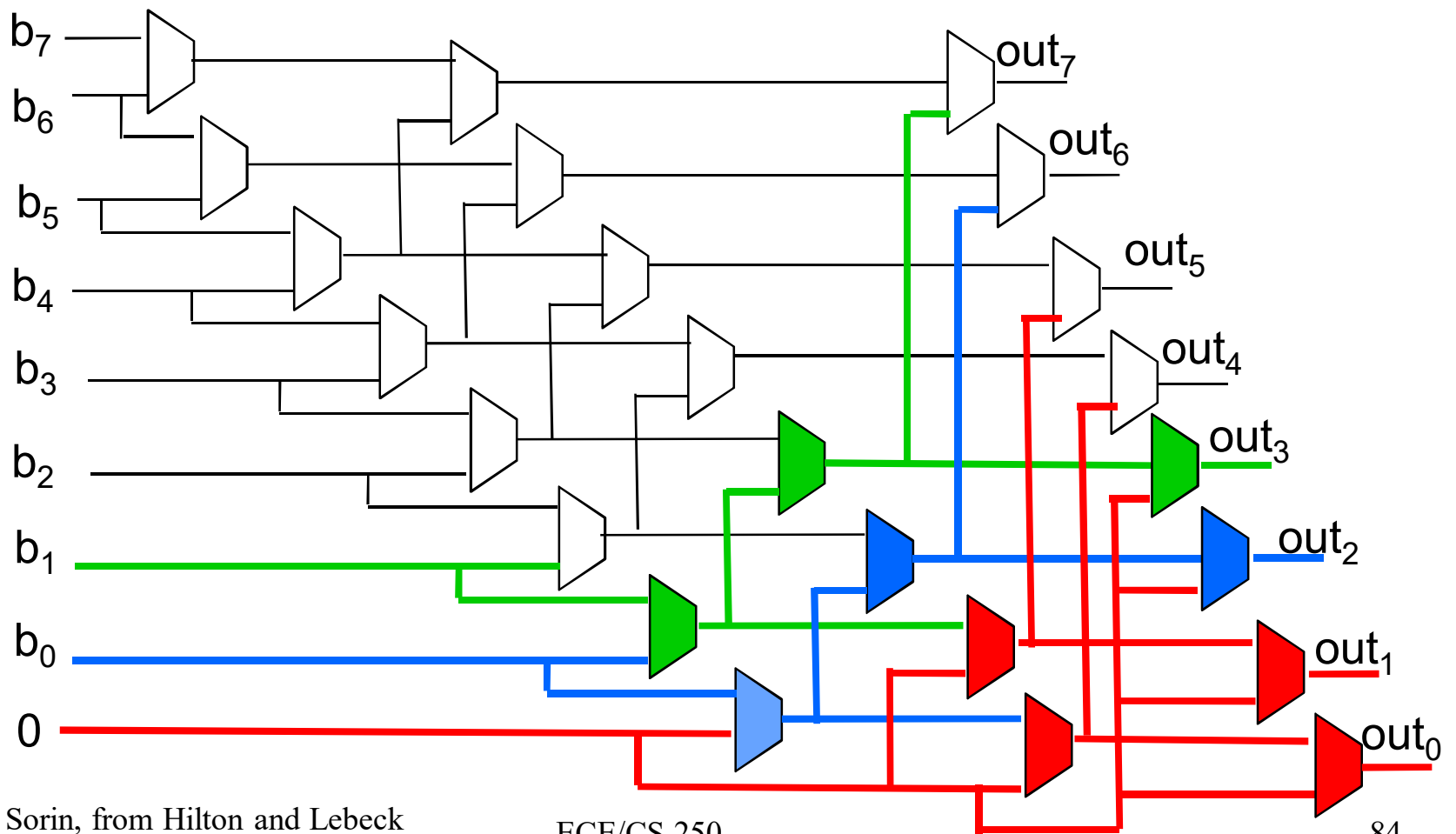- **Shifter in action: shift by 010 ($=2_{10}$)**
 - From L to R: S = 0, 1, 0




Now shifted by 3-bit number

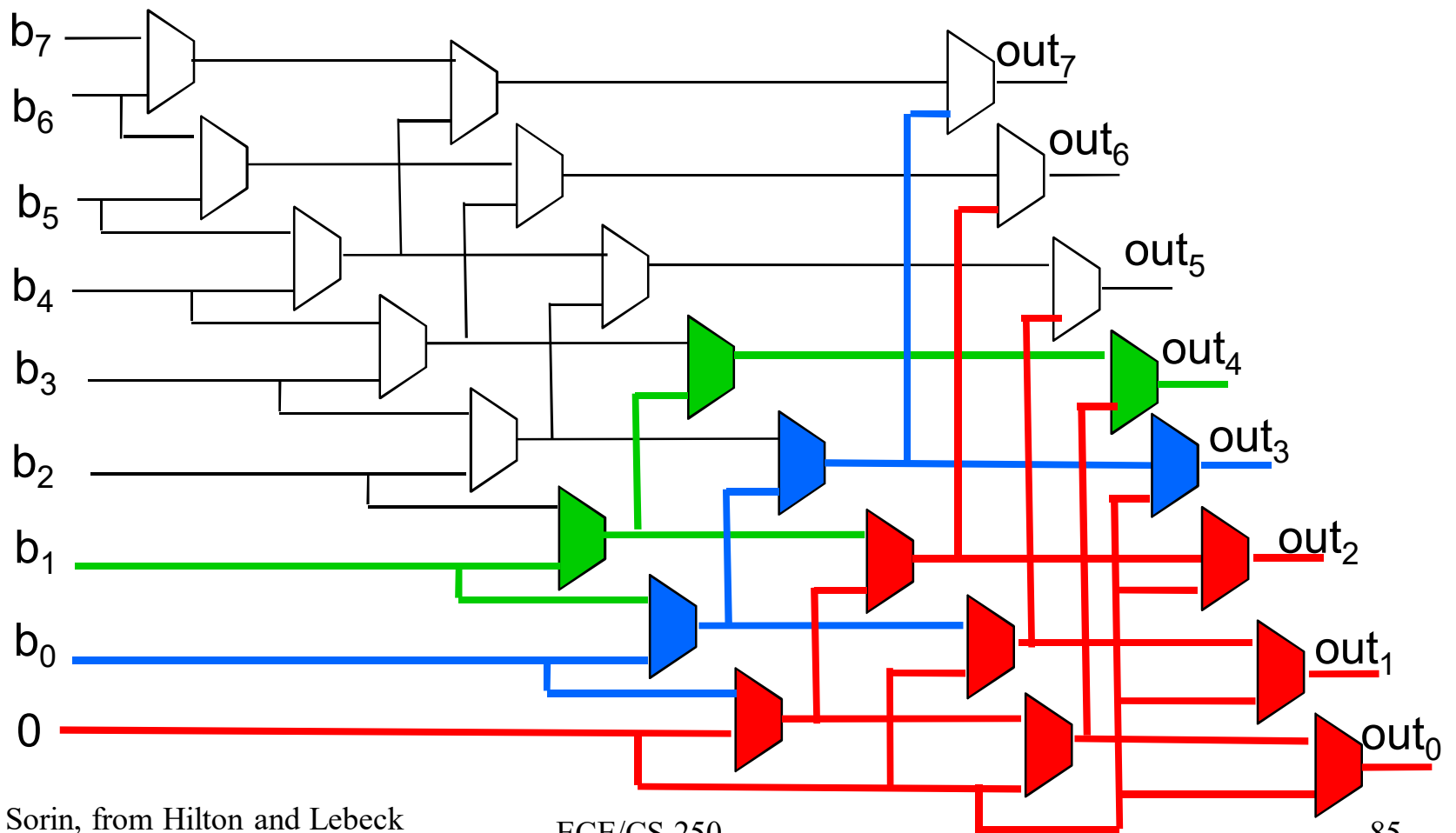
- **Shifter in action: shift by 011**
 - From L to R: S= 1, 1, 0 (reverse of shift amount)



Barrel Shifter

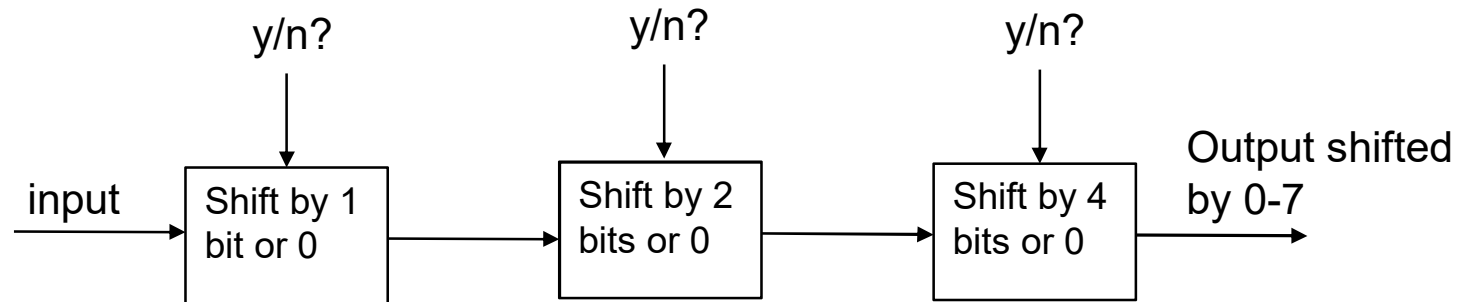

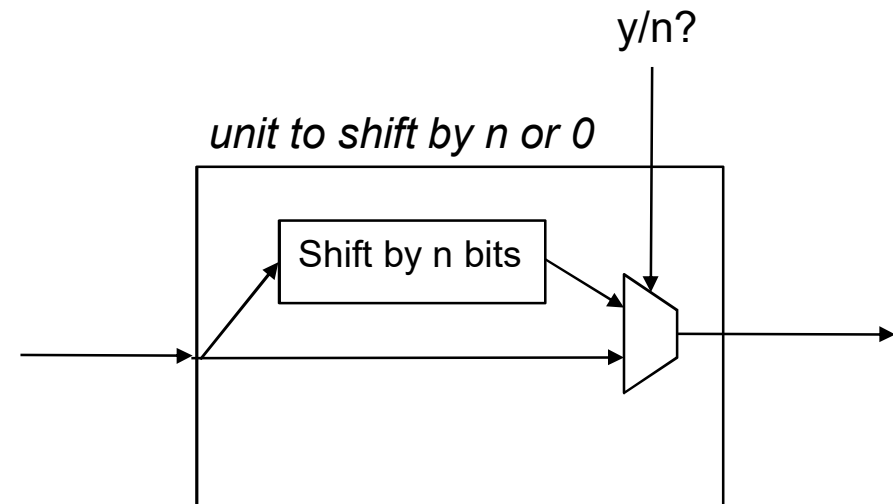There are three control inputs (y/n).
Any value from 0-7 can be
achieved with them (000-111).



Summary

- **Boolean Algebra & functions**
- **Logic gates (AND, OR, NOT, etc)**
- **Multiplexors**
- **Adder**
- **Arithmetic Logic Unit (ALU)**