

## ECE/CS 250: Computer Architecture

### Combinational Logic: Boolean Algebra, Logic Gates


Copyright Daniel Sorin  
Duke University

Slides are derived from work by  
Drew Hilton (Duke), Alvy Lebeck (Duke), Amir  
Roth (Penn)

## Reading

- Appendix B (parts 1,2,3,5,6,7,8,9,10)
- This material is covered in MUCH greater depth in ECE/CS 350 – please take ECE/CS 350 if you want to learn enough digital design to build your own processor

## What We've Done, Where We're Going

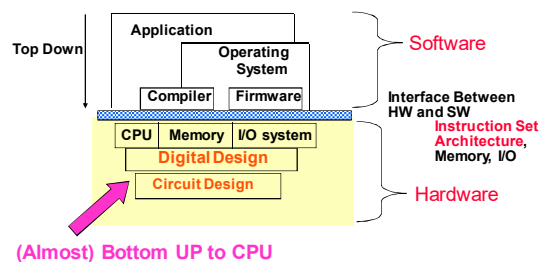

## Computer = Machine That Manipulates Bits

- Everything is in binary (bunches of 0s and 1s)
  - Instructions, numbers, memory locations, etc.
- Computer is a machine that operates on bits
  - Executing instructions → operating on bits
- Computers physically made of **transistors**
  - Electrically controlled switches
- We can use transistors to build logic
  - E.g., if this bit is a 0 and that bit is a 1, then set some other bit to be a 1
  - E.g., if the first 5 bits of the instruction are 10010 then set this other bit to 1 (to tell the adder to subtract instead of add)

## How Many Transistors Are We Talking About?

### Pentium III

- Processor Core 9.5 Million Transistors

• Total: 28 Million Transistors

### Pentium 4

- Total: 42 Million Transistors

### Core2 Duo (two processor cores)

- Total: 290 Million Transistors

### Core2 Duo Extreme (4 processor cores, 8MB cache)

- Total: 590 Million Transistors

### Core i7 with 6-cores

- Total: 2.27 Billion Transistors

How do they design such a thing? Carefully!

## Abstraction!

- Use of **abstraction** (key to design of any large system)
  - Put a few (2-8) transistors into **logic gate** (OR, AND, XOR, ...)
  - Combine gates into logical functions (add, select,...)
  - Combine adders, shifters, etc., together into modules
    - Units with well-defined interfaces for large tasks: e.g., decode
  - Combine a dozen of those into a core...
  - Stick 4 cores on a chip...

## You are here:

- Use of **abstraction** (key to design of any large system)
  - Put a few (2-8) transistors into a **logic gate**
  - **Combine gates into logical functions (add, select,...)**
  - Combine adders, muxes, etc together into modules  
Units with well-defined interfaces for large tasks: e.g., decode
  - Combine a dozen of those into a core...
  - Stick 4 cores on a chip...

## Boolean Algebra

- **First step to logic: Boolean Algebra**
  - Manipulation of True / False (1/0)
  - After all: everything is just 1s and 0s
- **Given inputs (variables): A, B, X, P, Q...**
  - Compute outputs using logical operators, such as:
- **NOT:**  $\neg A$  ( $= \sim A = \bar{A}$ )
- **AND:**  $A \& B$  ( $= A \cdot B = A * B = AB = A \wedge B$ ) =  $A \& B$  in C/C++
- **OR:**  $A \mid B$  ( $= A + B = A \vee B$ ) =  $A \mid\mid B$  in C/C++
- **XOR:**  $A \wedge B$  ( $= A \oplus B$ )
- NAND, NOR, XNOR, Etc.

## Truth Tables

- Can represent as **Truth Table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

## Truth Tables

- Can represent as **truth table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND (a,b)
0	0	0
0	1	0
1	0	0
1	1	1

## Truth Tables

- Can represent as **truth table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND (a,b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR (a,b)
0	0	0
0	1	1
1	0	1
1	1	1

## Truth Tables

- Can represent as **truth table**: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND (a,b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR (a,b)
0	0	0
0	1	1
1	0	1
1	1	1

a	b	XOR (a,b)
0	0	0
0	1	1
1	0	1
1	1	0

a	b	NAND (a,b)
0	0	1
0	1	1
1	0	1
1	1	0

a	b	NOR (a,b)
0	0	1
0	1	0
1	0	0
1	1	0

### Any Inputs, Any Outputs

- Can have any # of inputs, any # of outputs
- Can have arbitrary functions:

a	b	c	$f_1, f_2$
0	0	0	0 1
0	0	1	1 1
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	0	1	1 1
1	1	0	0 1
1	1	1	1 1

### Let's Write a Truth Table for a Function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

A	B	C	Output

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

A	B	C	Output
0	0	0	

Fill in Inputs  
Counting in Binary

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

A	B	C	Output
0	0	0	
0	0	1	

Fill in Inputs  
Counting in Binary

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

A	B	C	Output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Fill in Inputs  
Counting in Binary

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

A	B	C	Output
0	0	0	1
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Fill in Inputs  
Counting in Binary

Compute Output  
 $(0 \& 0) \mid !0 = 0 \mid 1 = 1$

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

Fill in Inputs  
Counting in Binary

Compute Output  
 $(0 \& 0) \mid !1 = 0 \mid 0 = 0$

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

Fill in Inputs  
Counting in Binary

Compute Output  
 $(0 \& 1) \mid !0 = 0 \mid 1 = 1$

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

### Let's write a Truth Table for a function...

- Example:  
 $(A \& B) \mid !C$

Start with Empty TT  
Column Per Input  
Column Per Output

Fill in Inputs  
Counting in Binary

Compute Output

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

### You try one...

- Try one yourself (take 2 minutes):  
 $(!A \mid B) \& !C$

### Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm..

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm ...

Could write down every "true" case  
Then OR together:

$(!A \& !B \& !C) \mid$   
 $(!A \& !B \& C) \mid$   
 $(!A \& B \& !C) \mid$   
 $(A \& B \& !C) \mid$   
 $(A \& B \& C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm..

Could write down every “true” case

Then OR together:

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$   
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$   
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- Given a Truth Table, find the formula?

Hmmm..

Could write down every “true” case

Then OR together:

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$   
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$   
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- This approach is called “sum of products”
  - Works every time
  - Result is right...
  - But really ugly

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$   
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$   
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ C)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- This approach: “sum of products”
  - Works every time
  - Result is right...
  - But really ugly

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$   
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$   
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B \ \& \ C)$

Could just be  $(A \ \& \ B)$  here ?

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- This approach: “sum of products”
  - Works every time
  - Result is right...
  - But really ugly

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$   
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$   
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Suppose I turn it around...

- This approach: “sum of products”
  - Works every time
  - Result is right...
  - But really ugly

$(\neg A \ \& \ \neg B \ \& \ \neg C) \mid$   
 $(\neg A \ \& \ \neg B \ \& \ C) \mid$   
 $(\neg A \ \& \ B \ \& \ \neg C) \mid$   
 $(A \ \& \ B)$

Could just be  $(\neg A \ \& \ \neg B)$  here

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

**Suppose I turn it around...**

- This approach: “sum of products”
  - Works every time
  - Result is right...
  - But really ugly

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

```
(!A & !B) |
(!A & B & !C) |
(A&B)
```

Looks nicer...

Can we do better?

**Suppose I turn it around...**

- **This approach: “sum of products”**
  - Works every time
  - Result is right...
  - But really ugly

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(!A & !B) |  
(!A & B & !C) |  
(A&B)

**This has a lot in common:**  
**!A & (something)**

**Suppose I turn it around...**

- This approach: “sum of products”
  - Works every time
  - Result is right...
  - But really ugly

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$(\neg A \ \& \ \neg (B \ \& \ C)) \mid (A \ \& \ B)$$

Just did some of these by intuition.. but

- Somewhat intuitive approach to simplifying
- This is **math**, so there are formal rules
  - Just like “regular” algebra

## Boolean Function Simplification

- Boolean expressions can be simplified by using the following rules (bitwise logical):
 

$\neg A \ \& \ A = A$	$A \mid \neg A = A$
$\neg A \ \& \ 0 = 0$	$A \mid 0 = A$
$\neg A \ \& \ 1 = A$	$A \mid 1 = 1$
$\neg A \ \& \ !A = 0$	$A \mid !A = 1$
- $!!A = A$
- $\&$  and  $\mid$  are both commutative and associative
- $\&$  and  $\mid$  can be distributed:  $A \ \& \ (B \mid C) = (A \ \& \ B) \mid (A \ \& \ C)$
- $\&$  and  $\mid$  can be subsumed:  $A \mid (\neg A \ \& \ B) = A$

$$\begin{array}{l} A \mid A = A \\ A \mid 0 = A \\ A \mid 1 = 1 \\ A \mid !A = 1 \end{array}$$

## DeMorgan's Laws

- **Two (less obvious) Laws of Boolean Algebra:**
    - Let's push negations inside, flipping & and |
- $$\neg (A \ \& \ B) = (\neg A) \ | \ (\neg B)$$
- $$\neg (A \ | \ B) = (\neg A) \ \& \ (\neg B)$$
- You should try this at home – build truth tables for both the left and right sides and see that they're the same

### Using DeMorgan on Early Example

$(\neg A \ \& \ \neg (B \ \& \ C)) \mid$   
 $(A \ \& \ B)$   
 =  
 $(\neg A \ \& \ (\neg B \mid \neg C)) \mid$   
 $(A \ \& \ B)$

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

### Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$

### Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$   
 DeMorgan's  
 $\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$

### Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$   
 DeMorgan's  
 $\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$   
 Double Negation Elimination  
 $A \ \& \ (A \ \& \ (B \mid C))$

### Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$   
 DeMorgan's  
 $\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$   
 Double Negation Elimination  
 $A \ \& \ (A \ \& \ (B \mid C))$   
 Associativity of &  
 $(A \ \& \ A) \ \& \ (B \mid C)$

### Simplification Example:

$\neg (\neg A \mid \neg (A \ \& \ (B \mid C)))$   
 DeMorgan's  
 $\neg \neg A \ \& \ \neg \neg (A \ \& \ (B \mid C))$   
 Double Negation Elimination  
 $A \ \& \ (A \ \& \ (B \mid C))$   
 Associativity of &  
 $(A \ \& \ A) \ \& \ (B \mid C)$   
 $A \ \& \ A = A$   
 $A \ \& \ (B \mid C)$

### You try this:

Come up with a formula for this Truth Table  
Simplify as much as possible

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

### Something That Trips Up Students

$!A \& !B$  is not the same as  $!(AB)$

Students tend to notice this when it's written this way  
but NOT when it's written with lines above the terms:

$$\overline{A} \cdot \overline{B} \neq \overline{AB}$$

"Not A and Not B" is not the same as "Not AB"

The former is true if  $(A,B) = (0,0)$ .

The latter is true if  $(A,B) = (0,0)$  or  $(0,1)$  or  $(1,0)$ .








### Applying the Theory

- Lots of good theory
- Can reason about complex Boolean expressions
- But why is this useful? (fun party trick)

### Boolean Gates

- **Gates** are electronic devices that implement simple Boolean functions (building blocks of hardware)

#### Examples

       

### Guide to Remembering your Gates

- This one looks like it just points its input where to go
  - It just produces its input as its output
  - Called a buffer




### Guide to Remembering your Gates

- This one looks like it just points its input where to go
  - It just produces its input as its output
  - Called a buffer




- A circle always means negate (invert)

 




## Brief Interlude: Building An Inverter

 


This is not on the test.
 
## Guide to Remembering Your Gates

- AND Gates have a straight edge, like an A (in AND)




 - OR Gates have a curved edge, like an O (in OR)



## Guide to Remembering Your Gates


- If we stick a circle on them...

 

- We get NAND (NOT-AND) and NOR (NOT-OR)
  - $\text{NAND}(a, b) = \text{NOT}(\text{AND}(a, b))$
 
## Guide to Remembering Your Gates

- XOR looks like OR (curved line)
  - But has two lines (like an X does)




- Can put a dot for XNOR
  - XNOR is 1-bit "equals" by the way



## Boolean Functions, Gates and Circuits


- **Circuits** are made from a network of gates.

$(!A \ \& \ !C) \mid (A \ \& \ C)$

 
 
## A few more words about gates

- Gates have inputs and outputs
  - If you try to hook up two outputs, bad things happen (your processor catches fire)



- If you don't hook up an input, it behaves kind of randomly (also not good, but not set-your-chip-on-fire bad)

### Let's Make a Useful Circuit

- Pick between 2 inputs (called 2-to-1 MUX)
  - Short for multiplexor
- What might we do first?

### Let's Make a Useful Circuit

- Pick between 2 inputs (called 2-to-1 MUX)
  - Short for multiplexor
- What might we do first?
  - Make a truth table?
    - S is selector:
      - S=0, pick A
      - S=1, pick B

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

### Let's Make a Useful Circuit

- Pick between 2 inputs (called 2-to-1 MUX)
  - Short for multiplexor
- What might we do first?
  - Make a truth table?
    - S is selector:
      - S=0, pick A
      - S=1, pick B
  - Next: sum-of-products
    - $(\neg A \ \& \ B \ \& \ S) \mid$
    - $(A \ \& \ \neg B \ \& \ \neg S) \mid$
    - $(A \ \& \ B \ \& \ \neg S) \mid$
    - $(A \ \& \ B \ \& \ S)$

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

### Let's Make a Useful Circuit


- Pick between 2 inputs (called 2-to-1 MUX)
  - Short for multiplexor
- What might we do first?
  - Make a truth table?
    - S is selector:
      - S=0, pick A
      - S=1, pick B
  - Next: sum-of-products
    - $(A \ \& \ \neg S) \mid$
    - $(B \ \& \ S)$
  - Simplify

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 
### Circuit Example: 2x1 MUX

Draw it in gates:


$$\text{MUX}(A, B, S) = (A \ \& \ \neg S) \mid (B \ \& \ S)$$



So common, we give it its own symbol:

 


### Example 4x1 MUX

 


## Arithmetic and Logical Operations in ISA

- What operations are there?
- How do we implement them?
  - Consider a 1-bit Adder

## A 1-bit Full Adder

 


## Example: 4-bit adder

 

## Subtraction





- How do we perform integer subtraction?
- What is the hardware?
  - Recall: hardware was why 2's complement was good idea
- Remember: Subtraction is just addition
  - $X - Y =$
  - $X + (-Y) =$
  - $X + (\sim Y + 1) =$

## Example: Adder/Subtractor

 
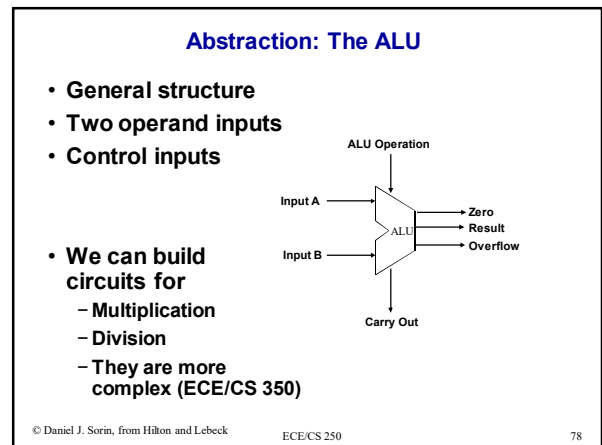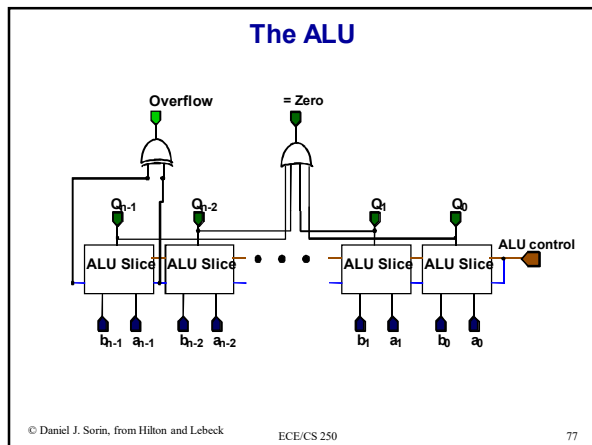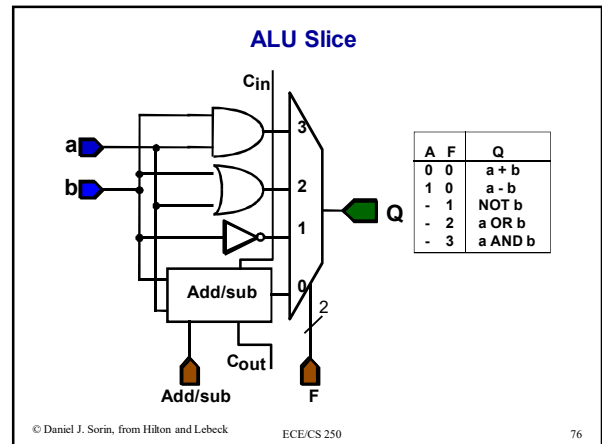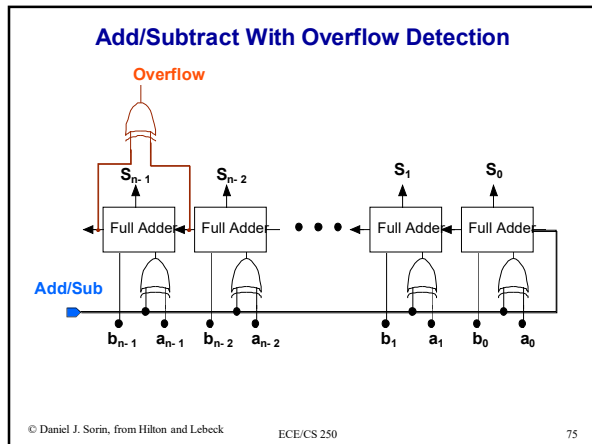
## Overflow


- We can detect unsigned overflow by looking at *CO*
- How would we detect signed overflow?
  - If adding positive numbers and result "is" negative
  - If adding negative numbers and result "is" positive
  - At most significant bit of adder, check if *C<sub>I</sub>* != *CO*
  - Can check with XOR gate


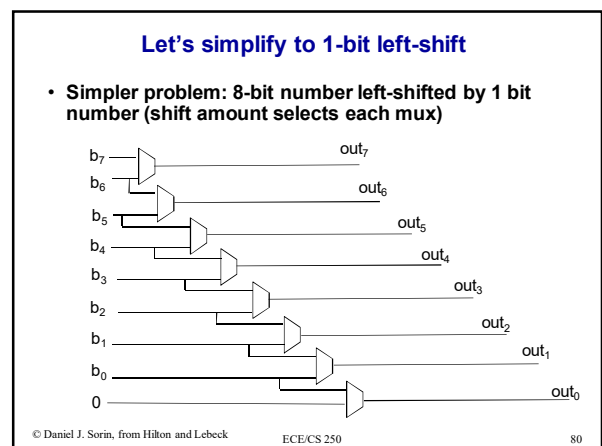
### Another Operation We Might Want: Shift


- Remember the  $\ll$  and  $\gg$  operations?
  - Shift left/shift right?
  - How would we implement these?
- Suppose you have an 8-bit number  $b_7b_6b_5b_4b_3b_2b_1b_0$
- And you can shift it left by a 3-bit number  $s_2s_1s_0$
- Option 1: Truth Table?
  - $2^{11} = 2048$  rows? Yuck.

© Daniel J. Sorin, from Hilton and Lebeck ECE/CS 250 79


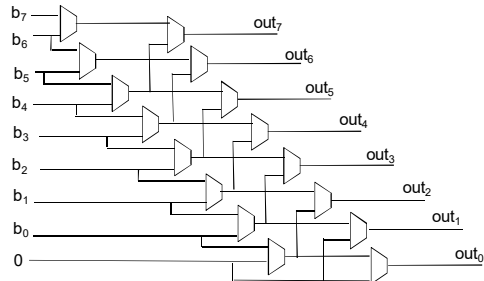
### Let's simplify to 2-bit left shift

- **Simpler problem: 8-bit number left-shifted by 2 bit number (i.e., can left-shift by 0, 1, 2, or 3)**




© Daniel J. Sorin, from Hilton and Lebeck

ECE/CS 250

81
 
### Now left-shifted by 3-bit number

- **Full problem: 8-bit number left-shifted by 3 bit number (can shift by 0-7 bits)**




© Daniel J. Sorin, from Hilton and Lebeck

ECE/CS 250

82
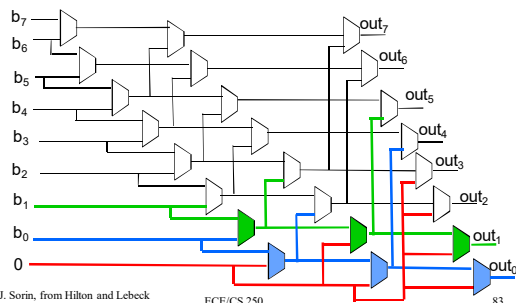
### Now shifted by 3-bit number

- **Shifter in action: shift by 000 (all muxes have S=0)**




© Daniel J. Sorin, from Hilton and Lebeck

ECE/CS 250

83
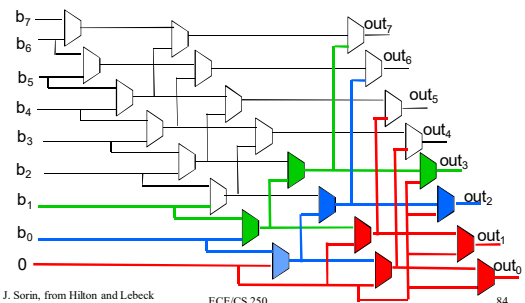
### Now shifted by 3-bit number

- **Shifter in action: shift by 010 (=2<sub>10</sub>)**  
– From L to R: S = 0, 1, 0




© Daniel J. Sorin, from Hilton and Lebeck

ECE/CS 250

84
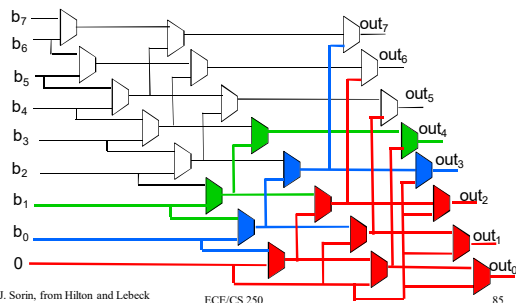
### Now shifted by 3-bit number

- **Shifter in action: shift by 011**  
– From L to R: S = 1, 1, 0 (reverse of shift amount)




© Daniel J. Sorin, from Hilton and Lebeck


ECE/CS 250

85

### Barrel Shifter

 

 There are three control inputs (y/n).  
Any value from 0-7 can be achieved with them (000-111).



© Daniel J. Sorin, from Hilton and Lebeck

ECE/CS 250

86

## Summary

- Boolean Algebra & functions
- Logic gates (AND, OR, NOT, etc)
- Multiplexors
- Adder
- Arithmetic Logic Unit (ALU)